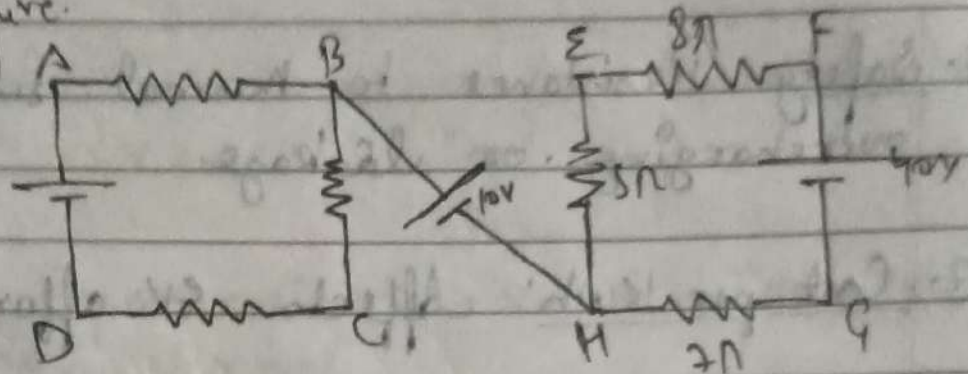


## ASSIGNMENT-2

Q1 Find the value of  $V_E$  &  $V_H$  in the given figure.



sol<sup>n</sup>. In loop EFGHE

$$I_A = \frac{40}{8+5+7} = \frac{40}{20} = 2A$$

$$V_F = 40V$$

$$\Rightarrow \text{Voltage across } 8\Omega = 16V$$

$$V_E = 40 - 16 = 24V$$

$$\Rightarrow \text{Voltage across } 7\Omega = 14V$$

$$V_H = 14V$$

In loop ABCDA

$$I_L = \frac{20}{6+5+9} = 1A$$

$$V_A = V_0 + 20$$

⇒ Voltage across  $6\Omega = 6V$

$$V_B = V_A - 6 = V_0 + 14$$

⇒ Voltage across  $9\Omega = 9V$

$$V_C = V_0 + 9$$

In branch BH

$$V_B - V_H = 10$$

$$V_B - 14 = 10 \Rightarrow V_B = 24V$$

$$V_H = V_0 + 14$$

$$24 = V_0 + 14 \Rightarrow V_0 = 10V$$

$$V_A = V_0 + 20 \Rightarrow 30V$$

$$V_C = V_0 + 9 = 19V$$

$$V_{CC} = V_C - V_H = 19 - 24 = -5V$$


$$V_{AG} = V_A - V_G = 30 - 0 = 30V$$



Date :

Page No. :

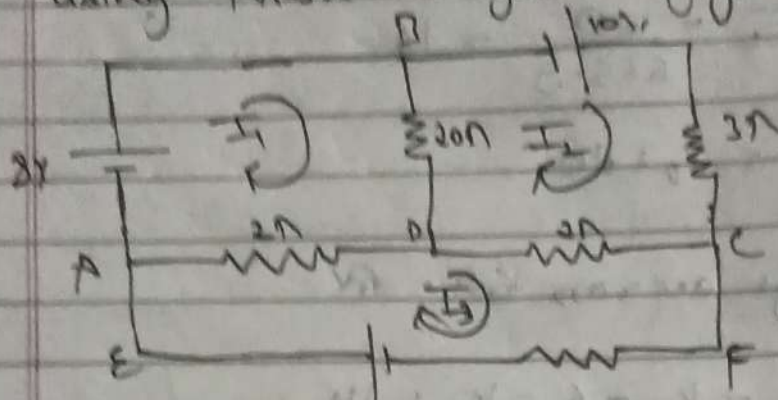Q. Find the current in  $5\Omega$  resistance using Mesh analysis in fig.



In mesh ADPA

$$(I_1 - I_2)2 + (I_1 - I_2)20 = 8$$

$$I_1 - I_2 + (I_1 - I_2)10 = 4$$

$$11I_1 - 10I_2 - I_3 = 4 \quad \text{--- (i)}$$

In mesh CDPC

$$I_2(3) + (I_2 - I_3)2 + (I_2 - I_1)20 = 10$$

$$3I_2 + 2I_2 - 2I_3 + 20I_2 - 20I_1 = 10$$

$$-20I_1 + 25I_2 - 2I_3 = 10 \quad \text{--- (ii)}$$

In Mesh ACFEA

$$(I_3 - I_1)2 + (I_3 - I_2)2 + I_3(5) = 12$$

$$2I_2 - 2I_1 + 3I_3 - 2I_2 + 5I_3 = 12$$


$$-2I_1 - 2I_2 + 8I_3 = 12 \quad \text{--- (iii)}$$

On solving eqn i, ii & iii

$$I_1 = 4.68 \text{ A}, I_2 = 4.41 \text{ A}, I_3 = 3.63 \text{ A}$$

$I_3$  passes through  $5\Omega$  resistor so current in  $5\Omega$  is  $3.63 \text{ A}$

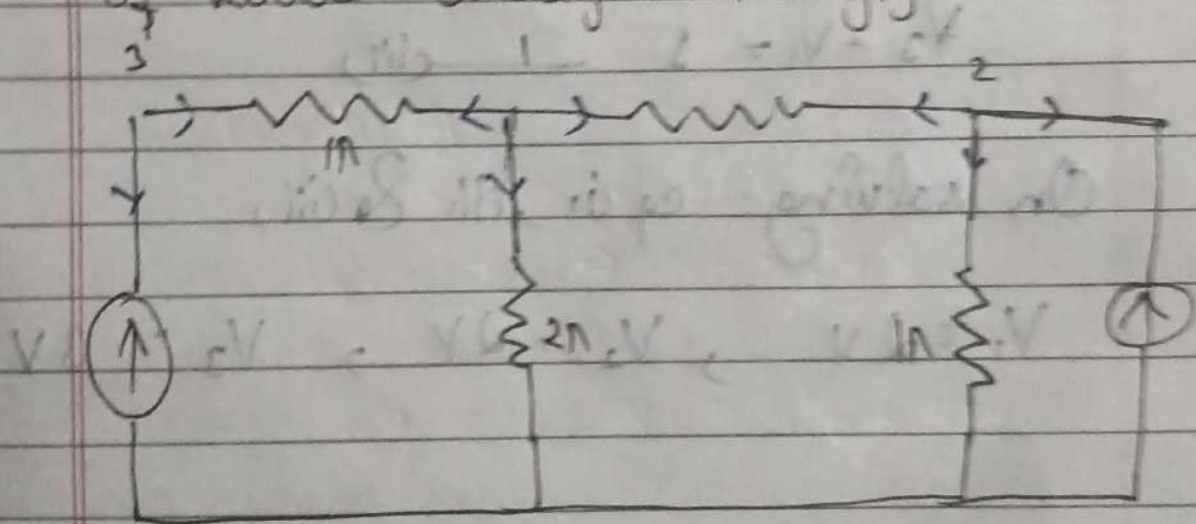Q3. Find the voltage  $V_1$  &  $V_2$  with the help of nodal analysis in figure.



\* At node 1

$$\frac{V_2 - V_1}{1} + \frac{V_1}{2} + \frac{V_1 - V_3}{2} = 0$$

$$\frac{2V_1 - 2V_3 + V_1 + V_1 + V_2}{2} = 0$$



$$4V_1 - V_2 - 2V_3 = 0 \quad \text{--- (i)}$$

At node 2.

$$\frac{V_2 - V_1}{2} - \frac{V_2}{1} - 2 = 0$$

$$3V_2 - V_1 - 4 = 0$$

$$3V_2 - V_1 = 4 \quad \text{--- (ii)}$$

At node 3.


$$-1 + \frac{V_3 - V_1}{1} = 0$$

$$V_3 - V_1 = 1 \quad \text{--- (iii)}$$

On solving eq (i), (ii) & (iii),

$$V_1 = 2V, \quad V_2 = 2V, \quad V_3 = 3V$$

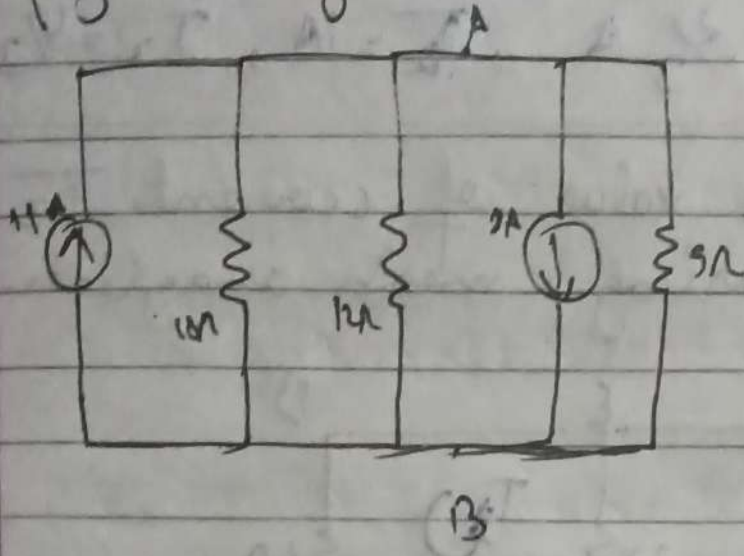Q4. Find the value of currents shown in fig. using nodal analysis.



At node A.

$$-11 + \frac{V}{18} + \frac{V}{12} - 9 + \frac{V}{9} = 0$$

$$\frac{V}{3} \left( \frac{1}{6} + \frac{1}{4} + \frac{1}{3} \right) - 3 = 0$$

$$\frac{V}{3} \left( \frac{2+3+4}{12} \right) = 3$$

$$V \left( \frac{9}{12} \right) = 9$$

$$V = 12 \text{ V}$$

$$\text{Now } I_1 = \frac{V}{18} = \frac{12}{18} = \frac{2}{3} \text{ A}$$


$$I_2 = \frac{V}{12} = \frac{12}{12} = 1 \text{ A}$$



$$I_3 = \frac{V}{R} = \frac{12}{9} = \frac{4}{3} \text{ A}$$

$$\text{So } I_1 = \frac{2}{3} \text{ A}, I_2 = 1 \text{ A}, I_3 = \frac{4}{3} \text{ A}$$

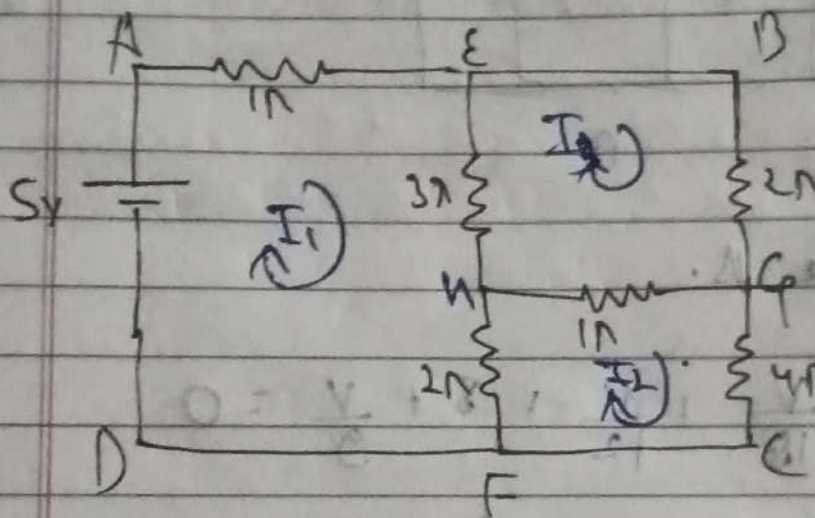Q5. Find the value of current  $I_3$  in figure using mesh analysis.



$\Rightarrow$   $I_1$  loop AEFDA

$$I_1(1) + (I_1 - I_2)3 + (I_1 - I_2)2 = 5$$

$$I_1 + 3I_1 - 3I_2 + 2I_1 - 2I_2 = 5$$

$$6I_1 - 2I_2 - 3I_3 = 5 \quad \text{--- (i)}$$

$I_2$  loop EBGHE

$$I_3(2) + (I_3 - I_1)1 + (I_3 - I_1) \times 1 = 0$$

$$2I_3 + I_3 - I_1 + 3I_3 - 3I_1 = 0$$

$$-3I_1 - I_1 + 6I_3 = 0 \quad \text{--- (ii)}$$

In loop 14 GCFH

$$(-I_2 - I_3)1 + I_2(4) + (I_2 - I_1)2 = 0$$

$$-I_2 - I_3 + 4I_2 + 2I_2 - 2I_1 = 0$$

$$-2I_1 + 7I_2 - I_3 = 0 \quad \text{--- (iii)}$$

On solving (i), (ii), & (iii)


$$I_1 = 1.39 \text{ A}, I_2 = 0.51 \text{ A}, I_3 = 0.823 \text{ A}$$

Q6. Find

i) The R.M.S Value

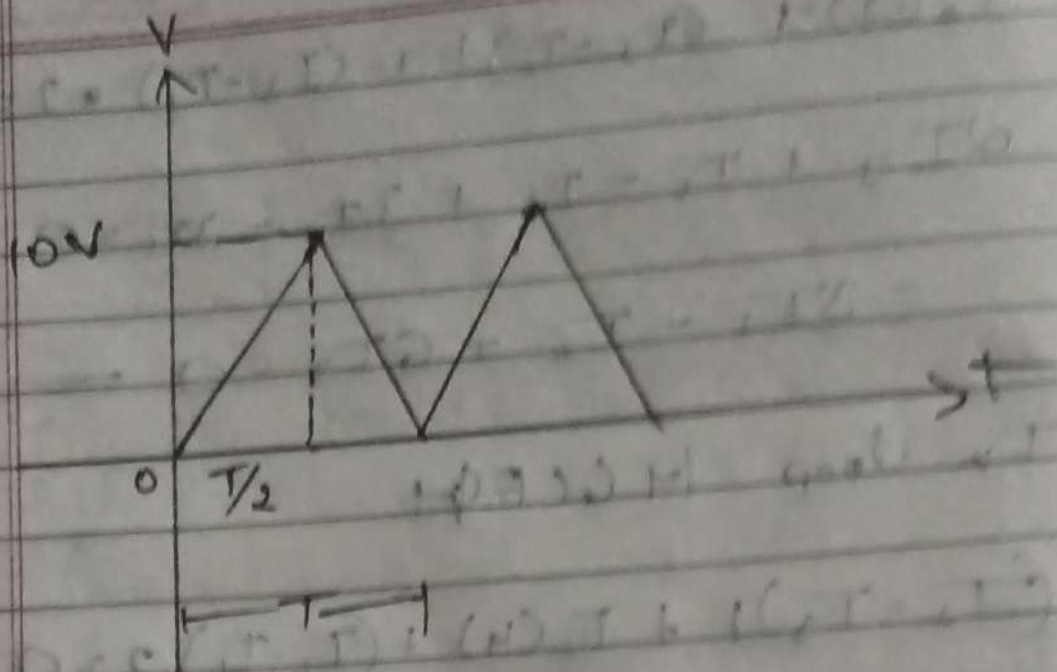ii) form factor for a symmetrical triangular wave.





At  $t=0$   $V=0$

At  $t=\frac{T}{2}$   $V=10V$

$$V(t) = 20 - \frac{20t}{T}$$

$$V_{avg} = \frac{1}{T} \int_0^T (20 - \frac{20t}{T}) dt$$

$$= \frac{20}{T} \left( \int_0^T dt - \int_0^T \frac{t}{T} dt \right)$$

$$= \frac{20}{T} \left[ t - \frac{t^2}{2T} \right]_0^T$$

$$= \frac{20}{T} \left[ \frac{T}{2} - \frac{T^2}{4T} \right]$$

$$= \frac{1}{T} \cdot \frac{20}{2} \left[ \frac{2T - T}{2} \right]$$

$$= \frac{5[2-1]}{1}$$

$$= 5V$$

$$\begin{aligned}
 i) \quad V_{rms} &= \sqrt{\frac{2}{T} \int_0^{T/2} v \cos \omega t \, dt} \\
 &= \sqrt{\frac{2}{T} \int_0^{T/2} \left(20 - \frac{20t}{T}\right)^2 dt} \\
 &= \sqrt{\frac{2 \cdot 20^2}{T} \int_0^{T/2} \left(1 - \frac{t}{T}\right)^2 dt} \\
 &= 20 \sqrt{\frac{2}{T} \int_0^{T/2} \left(1 + \frac{t^2}{T^2} - \frac{2t}{T}\right) dt} \\
 &= 20 \sqrt{\frac{2}{T} \left[ t + \frac{t^3}{3 \cdot T^2} - \frac{2t^2}{2T} \right]_0^{T/2}} \\
 &= 20 \sqrt{\frac{2}{T} \left[ \frac{T}{2} + \frac{T^3}{8 \cdot 3 \cdot T^2} - \frac{T^2}{4 \cdot T} \right]} \\
 &= 20 \sqrt{\frac{T^2}{T} \left( \frac{1}{2} + \frac{1}{24} - \frac{1}{4} \right)} \\
 &= 20 \sqrt{\frac{T}{24} (12 + 1 - 6)} \\
 &= \frac{20 \sqrt{7}}{\sqrt{24}} = 10 \sqrt{\frac{7}{3}} = 15.27
 \end{aligned}$$


$$ii) \quad F.F = \frac{V_{rms}}{V_{avg}} = \frac{15.27}{5} = 3.054$$



Q7. In the circuit shown in fig. Calculate

- i) Current  
ii) Voltage drops  $V_1, V_2, V_3$

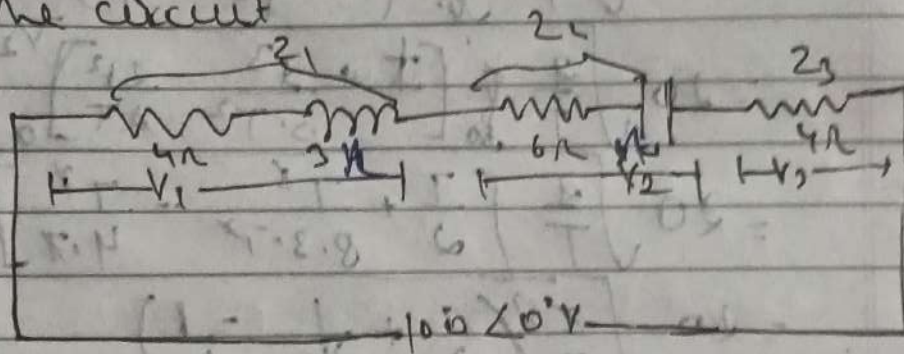- iii) Powers absorbed by each impedance & total power absorbed by the circuit



$$\therefore \begin{aligned} Z_1 &= (4 + j3) \\ Z_2 &= (6 - j8) \\ Z_3 &= 4 \end{aligned}$$

$$Z_T = 14 - j5 = 14.86 \angle -19.65^\circ$$


$$i) I = \frac{V}{Z_T} = \frac{100 \angle 0^\circ}{14.86 \angle -19.65^\circ} = 6.33 \angle 2.26^\circ$$

Q7. In the circuit shown in fig. Calculate

i) Current

ii) Voltage drops  $V_1$ ,  $V_2$ ,  $V_3$

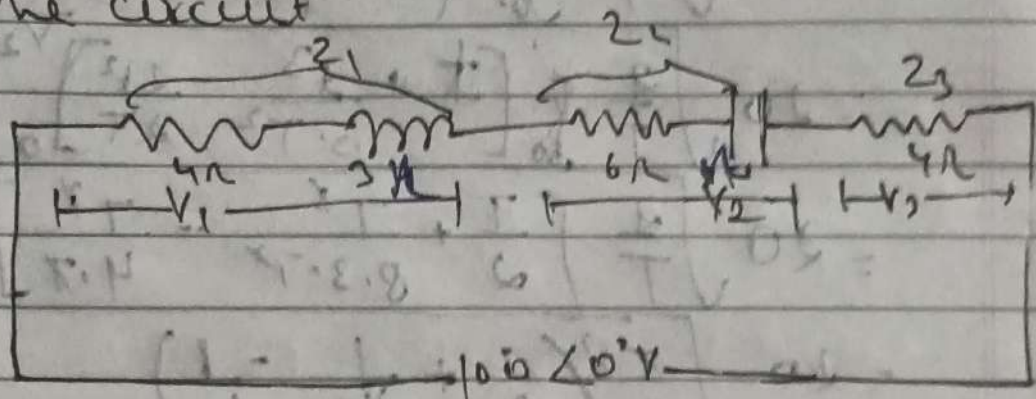iii) Powers absorbed by each impedance & total power absorbed by the circuit



$\therefore$   ~~$Z_1 = 4 + j3$~~

$$Z_1 = (4 + j3)$$

$$Z_2 = (6 - j1)$$

$$Z_3 = 4$$

$$Z_T = 14 - j1 = 14.86 \angle -19.65^\circ$$

$$i) I = \frac{V}{Z_T} = \frac{100 \angle 0^\circ}{14.86 \angle -19.65^\circ} = 6.33 \angle 2.26^\circ$$



$$\text{ii) } V_1 = I_2 = (6.33 + j2.26)(4 + j3) \\ = 18.54 + j28.03 \\ = 33.65 \angle 56.49^\circ \text{ V}$$

$$V_2 = I_2 = (6.33 + j2.26)(6 - j8) \\ = 19.9 - j64.2 \\ = 67.3 \angle -33.51^\circ \text{ V}$$

$$V_3 = I_2 = (6.33 + j2.26) \cdot 4 = 24.32 + j9.04 \\ = 26.32 \angle 19.62^\circ \text{ V}$$

$$\text{iii) } P_1 = |I|^2 R_1 = 180 \angle 80.706 \text{ W}$$

$$P_2 = |I|^2 R_2 = (45.1765) \cdot 6 = 271.039 \text{ W}$$

$$P_3 = |I|^2 R_3 = 180.706 \text{ W}$$

$$P_T = (P_1 + P_2 + P_3) = 180.706 + 271.039 + 180.706 \\ = 632.451 \text{ W}$$